

Calculation exercises

Exercise 1

- The duty cycle of boost converter is $D = 0.6$ and it is supplied from 12 V power source. What is the output voltage value?
- The input voltage of buck converter is 50 V and the output voltage is 35 V. What is the duty cycle D ?

Exercise 2

The buck converter is shown in Fig. 1. The converter operates in CCM, hence the inductor current is continuous.

- What kind of switching device is required? How it is controlled?
- Draw the current route in the circuit when the switch is conducting. Why the diode is not conducting at the same time?
- Draw the current route in the circuit when the switch is not conducting. Why the diode conducts this time?

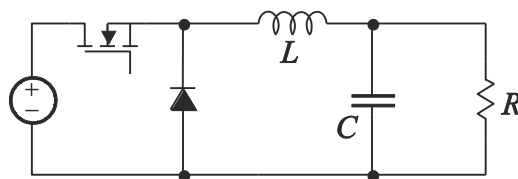


Fig. 1. Main circuit of buck converter

Exercise 3

The boost converter is shown in Fig. 2.

- Draw the main circuit diagram of the boost converter during the on- and off-times i.e. the switch is conducting or not conducting. The converter operates in CCM, hence the inductor current is continuous.
- Derive the equations for derivatives of inductor current and capacitor voltage during both conditions, on-time and off-time. Use Kirchhoff voltage- and current laws, the equation of inductor voltage $v_L = L \frac{di_L}{dt}$ and equation of capacitor current $i_C = C \frac{dv_C}{dt}$.
- Draw the inductor current waveform during one switching cycle. The converter operates in steady state (no start-up transient). Assume that capacitor voltage ripple is negligible. Mark the peak-to-peak inductor current ripple value to the figure.

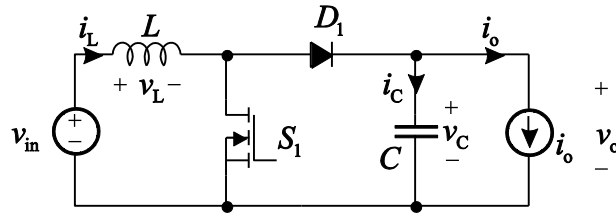


Fig. 2. Boost converter

Exercise 4

The duty cycle of the boost converter is 0.6 and it supplied from 12 V battery. The load requires 10 W power and the average inductor current value is 0.83 A. The switching frequency is 100 kHz.

- How large inductor is required for boost converter shown in Fig. 2 to limit the inductor current ripple Δi_L to be 20 % of the inductor current average value at maximum? Assume that capacitor voltage ripple is negligible. In addition, suppose that the inductor current varies linearly $di_L / dt = \Delta i_L / \Delta t$
- How the inductor current ripple change, if smaller inductor is used?

Exercise 5

The inductor current waveform of ideal boost converter is shown in Fig. 3a. The output voltage is 50V.

- What is the operating mode of the converter (CCM, DCM, BCM)?
- What is the duty cycle D value?
- What is the average input current value?
- What is the output voltage value?
- How large is the inductor L inductance value?
- What is the average output current value?


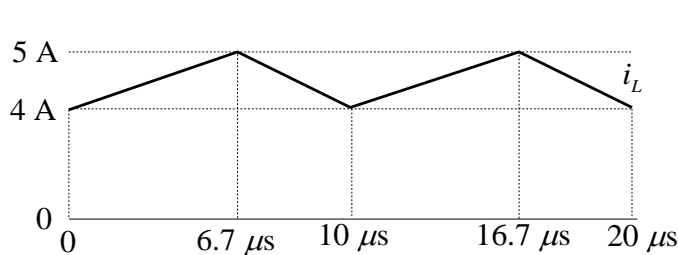


Fig 3. a) Inductor current waveform

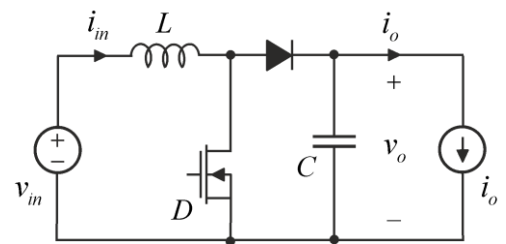

b) Boost converter

Exercise 6

Look at the boost converter shown in Exercise 5

- What is the MOSFET average current value?
- What is the MOSFET average voltage value?
- What is the diode average current value?
- What is the diode average voltage value?
- What is the capacitor average voltage value?

Exercise 7

The measured input current of an ideal buck converter is shown in Fig. 4 when the input voltage equals 10 V. Assume that capacitor voltage ripple is negligible. Compute

- The output voltage
- The switching frequency
- The size of the inductor

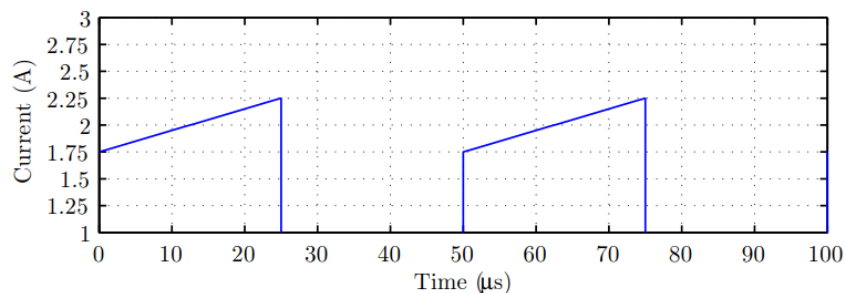


Fig. 4. Input current waveform

Exercise 8

In a diode-switched boost (step-up) converter shown in Fig. 3b consider all components to be ideal. Let input voltage be 12 V, output voltage 24 V, switching frequency 20 kHz and inductor $L = 260\mu\text{H}$. Does the converter operate always in continuous conduction mode (CCM) if output power $P_o \geq 50\text{W}$? Assume that capacitor voltage ripple is negligible.

Hint:

$$V_o = \frac{1}{1-D} V_{in}$$

$$v_L = L \frac{di_L}{dt}$$

$$R_{eq} = \frac{V_o}{I_o}$$

Exercise 9

Sketch the waveform of the diode voltage and diode current of the ideal boost converter analyzed in Exercise 8 when the output power equals 100 W. Based on the derived current waveform, compute the conduction power loss of the diode. Diode properties are $V_D = 0.7$ V and $r_D = 25$ m Ω (assume that the diode behaves as a series connection of a voltage source and a resistor during on-state).

Waveform	I _{rms}	I _{dc}	I _{ac(rms)}
	$\sqrt{D \left(I_p \times I_m + \frac{1}{3} (I_p - I_m)^2 \right)}$	$\frac{D (I_p + I_m)}{2}$	$\sqrt{I_{rms}^2 - I_{dc}^2}$