



Aspects on designing switched-mode power electronic converter for photovoltaic application

PhD Jenni Rekola
Tampere University of Technology
Finland
jenni.rekola@tut.fi



Co-funded by the
Erasmus+ Programme
of the European Union


Pulse-Width Modulation

- Controlling a dc-dc converter requires a steady pulse with adjustable width
- Usually a voltage signal
- Such method is referred as pulse-width-modulation or PWM
- Duty ratio is used to define the width of the pulse




$$D = \frac{t_{\text{on}}}{T_s}$$

$$t_{\text{on}} = DT_s$$

$$t_{\text{off}} = (1 - D)T_s = D'T_s$$

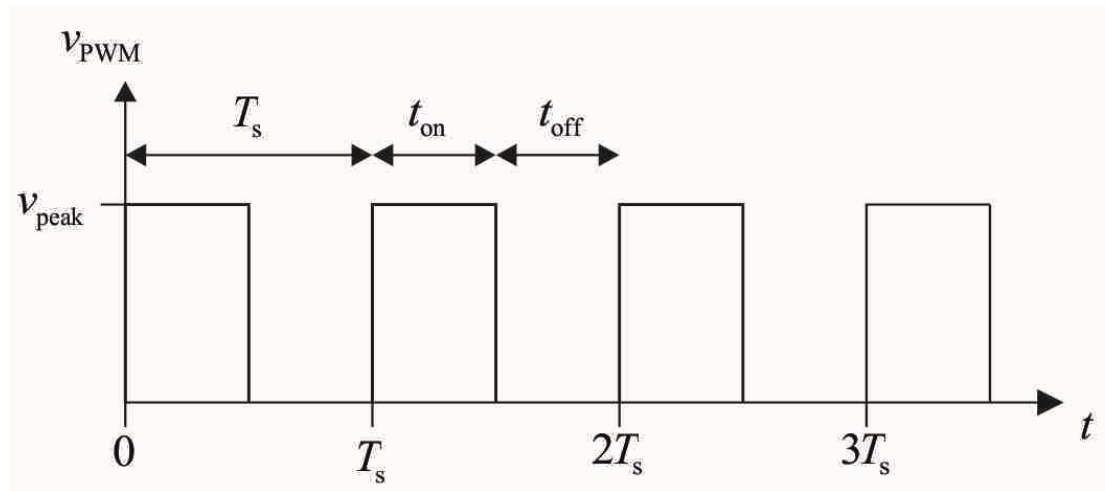

Pulse-Width Modulation

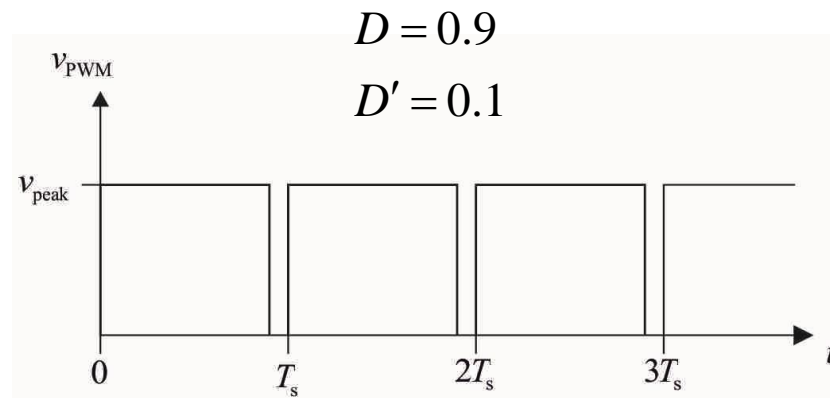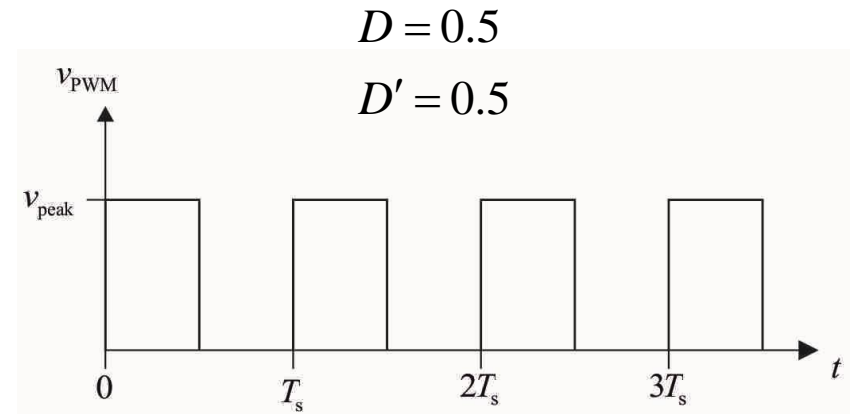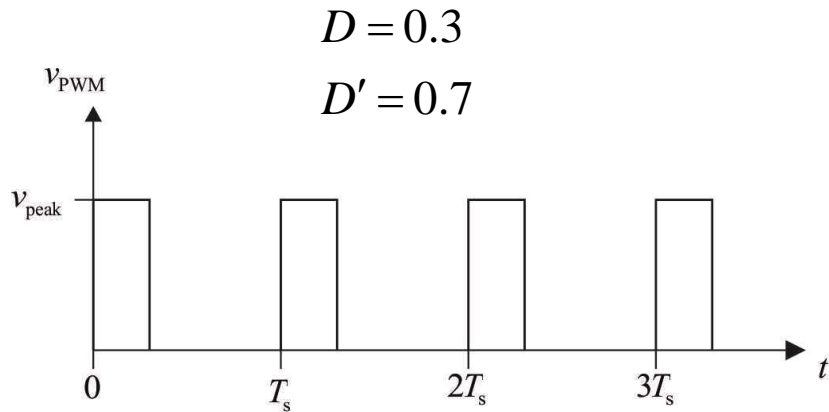


Pulse-Width Modulation

- The most common method to realize PWM is to compare a saw-tooth waveform with a control value
- External circuit is used to generate a voltage when the control voltage is larger than the saw-tooth waveform

$$v_{\text{control}} > v_{\text{tri}}$$

$$f_{\text{sw}} = \frac{1}{T_s}$$

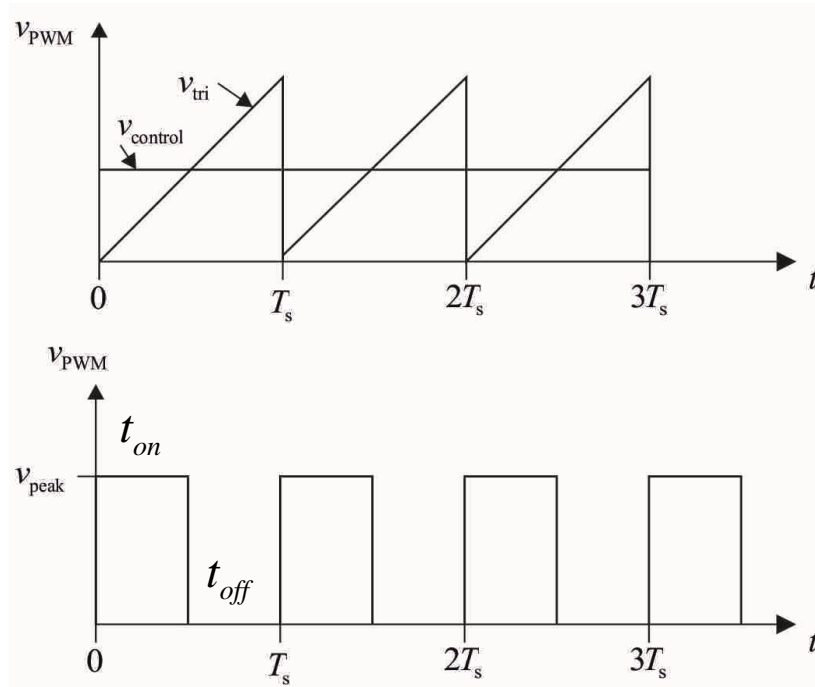


$$D = \frac{t_{\text{on}}}{T_s} = \frac{v_{\text{control}}}{\hat{v}_{\text{tri}}}$$




Pulse-Width Modulation (analog)

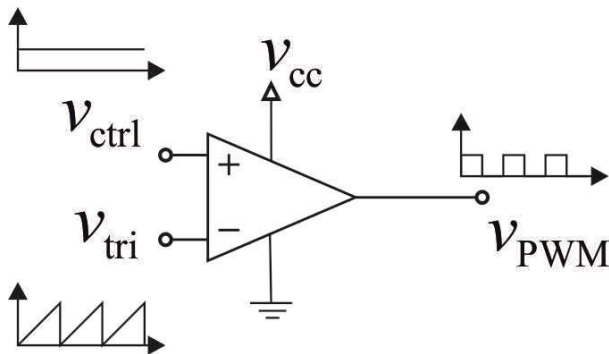- Comparison of two signals produces a pulse train
- Can be implemented using operational amplifier (comparator)




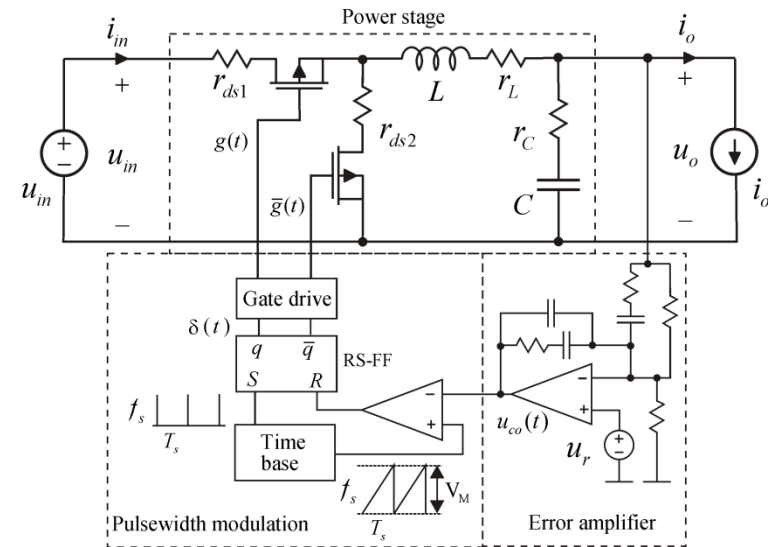
- Comparator switches its state between high and low
- Switching frequency depends on the saw-tooth waveform
- Width of the pulse depends on the dc level of the control signal




Picture: Professor Teuvo Suntio

Pulse-Width Modulation (digital)

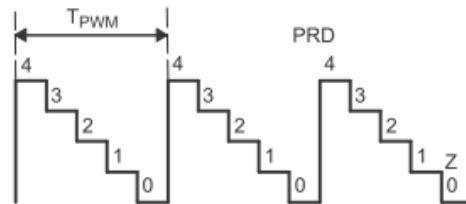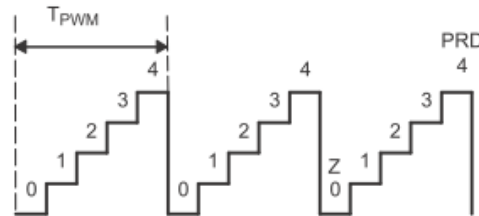- PWM and control system can be implemented digitally using a digital signal processor (DSP)
- PWM-waveforms can have several shapes inside the DSP



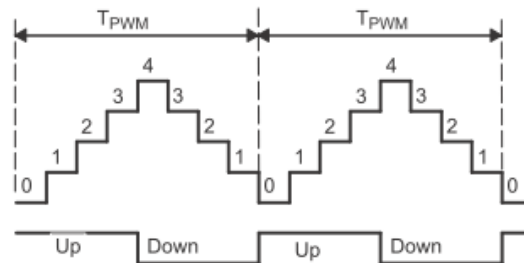For Up Count and Down Count
 $T_{PWM} = (TBPRD + 1) \times T_{TBCLK}$
 $F_{PWM} = 1 / (T_{PWM})$



For Up and Down Count
 $T_{PWM} = 2 \times TBPRD \times T_{TBCLK}$
 $F_{PWM} = 1 / (T_{PWM})$


CTR_dir

Up Down Up Down




Pulse-Width Modulation (digital)

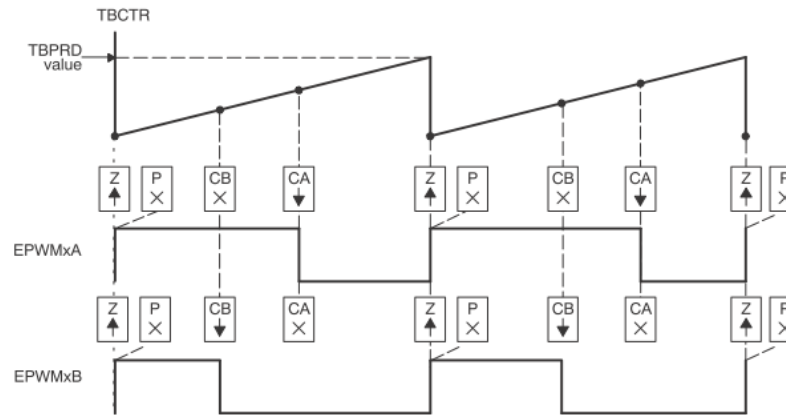- Output pin of the DSP is set to high state when compare value is less than the counter value → used in DC-DC converters



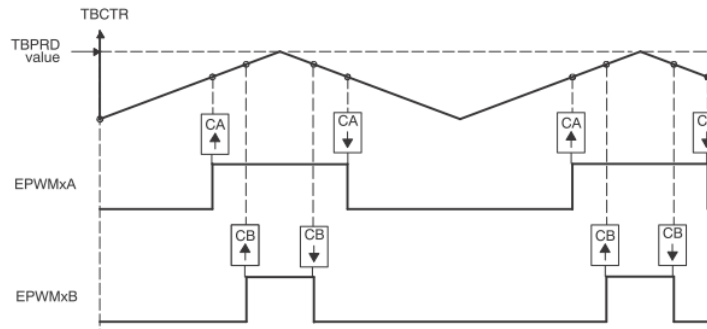- Counter can also generate a triangle waveform → used in DC-AC converters





Picture: Texas Instruments



Pulse-Width Modulation

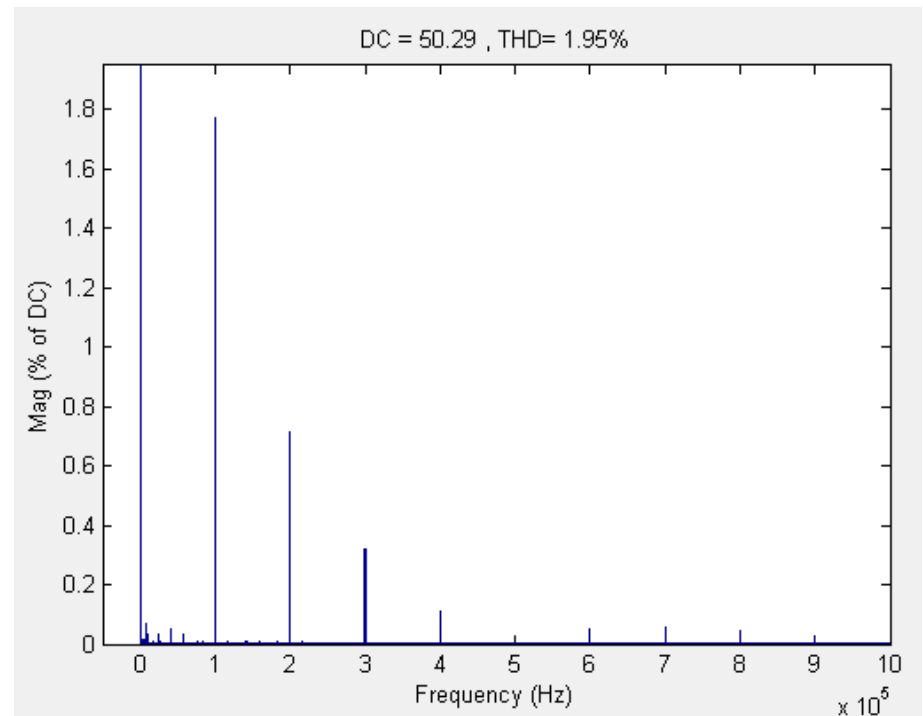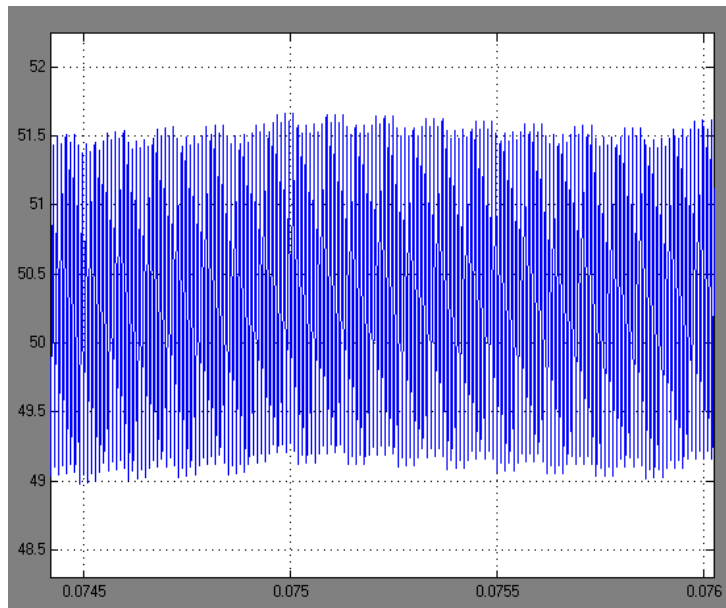- Produces high-frequency harmonics in converter currents and voltages
- Harmonics appear at the switching frequency and its multiples






Buck FFT-Analysis simulation example



Pulse-Width Modulation

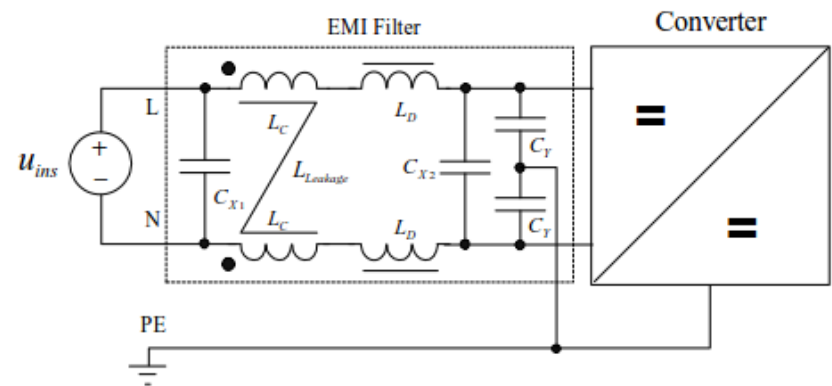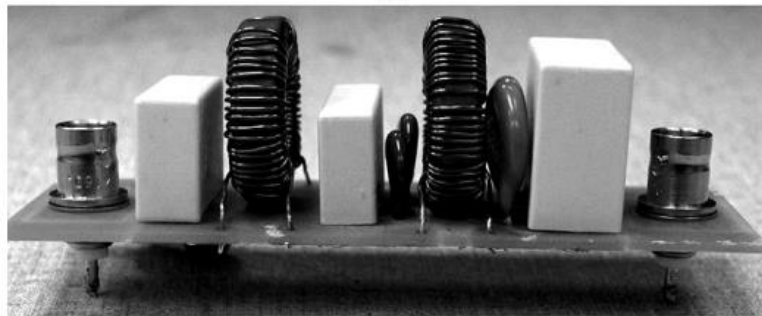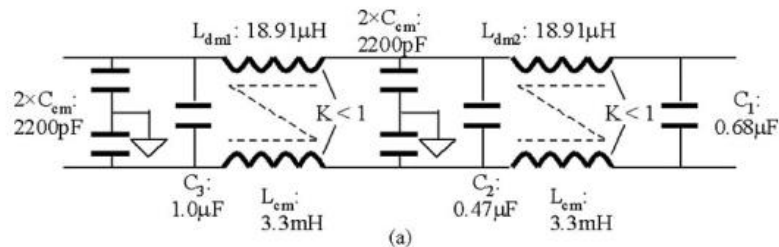- EMI-filters are required to filter out switching ripple




S. Wang et al, "Effects of Parasitic Parameters on EMI Filter Performance",
IEEE Trans. Power Electron., vol 19, no 3, pp. 869-877, 2004

Driver Circuit

- Driver circuit is needed to amplify the switch signal
- DSP / comparator cannot supply enough current to turn a transistor on
- Driver circuit has to supply or sink enough current to turn the switch on or off sufficiently fast

MCP1406/07


Functional Block Diagram⁽¹⁾

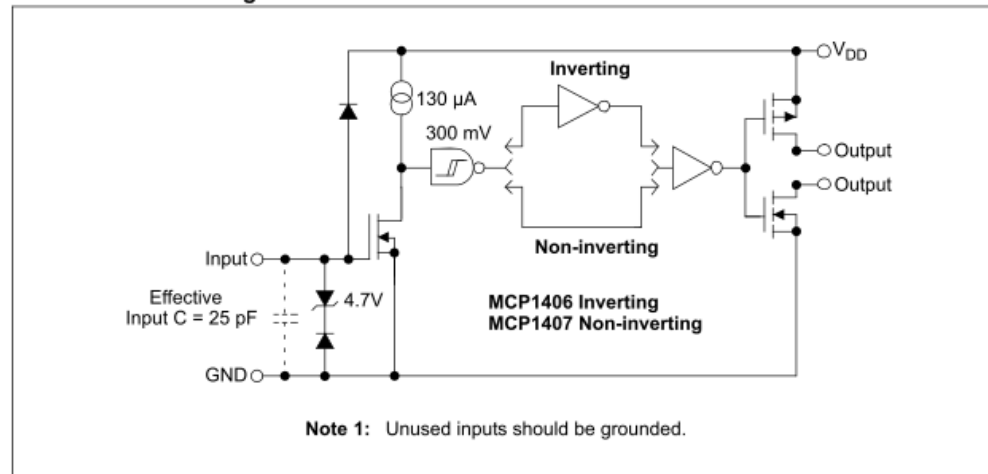

Driver Circuit

- Driver circuit has to be connected to supply voltage to operate
- Driver circuit can have also inverted output
- Comes in different sizes and cases

Package Types


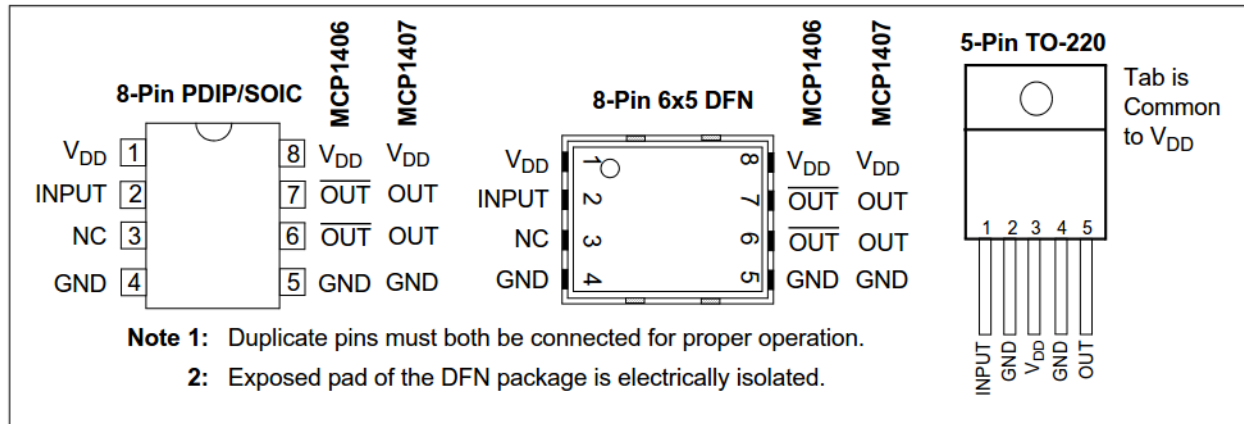


Example

Analyze the boost converter

The output voltage is 50V.

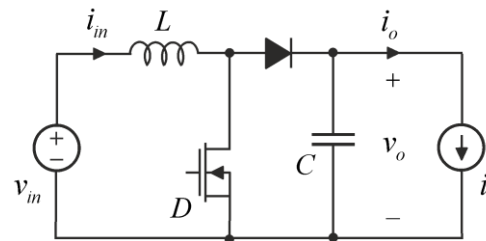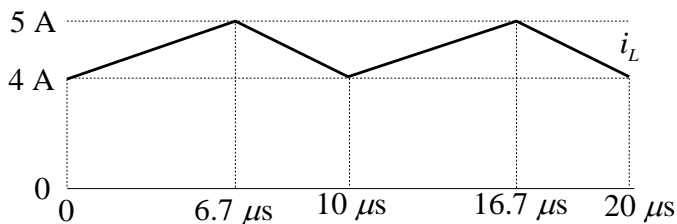- What is the MOSFET switching frequency?
- Draw the example of the converter PWM reference signal and the control signal
- How large is the inductor current ripple if the inductor value will be doubled?
- How large is the inductor current ripple if the switching frequency will be decreased to half?
- What is the power level of the converter?



Example solution

- a) What is the MOSFET switching frequency?

$$f_{sw} = \frac{1}{T_s} = \frac{1}{10\mu s} = 100kHz$$

- b) Draw the example of the converter PWM reference signal and the control signal
c) How large is the inductor current ripple if the inductor value will be doubled?

$$\hat{i}_{L-pp} = \frac{V_{in}}{L} \cdot DT_s = \frac{50V}{2 \cdot 335\mu H} \cdot 0,67 \cdot 10\mu s = 0,5A$$

- d) How large is the inductor current ripple if the switching frequency will be decreased to half?

$$\hat{i}_{L-pp} = \frac{V_{in}}{L} \cdot DT_s = \frac{50V}{2 \cdot 335\mu H} \cdot 0,67 \cdot 20\mu s = 1A$$

- e) What is the power level of the converter?


$$P_{in} = V_{in} I_{in} = 50V \cdot 4,5A = 225W$$



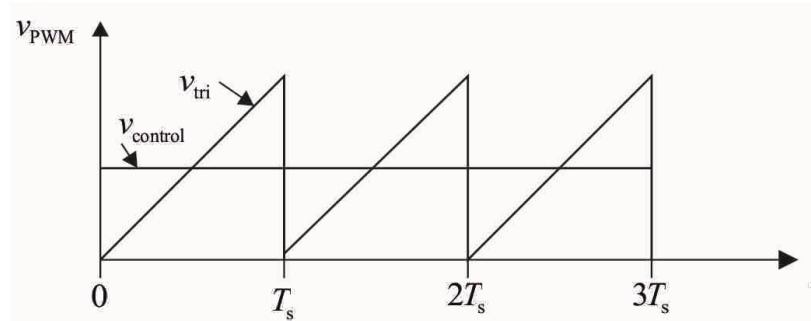
Example

The buck converter is controlled with PWM signal shown in the figure. The amplitude of the control signal is 1,2 V and the amplitude of the sawtooth-waveform is 3V. The switching cycle T_s is $10\mu\text{s}$. The input voltage of the converter is 50 V.

- What is the duty cycle D of the converter?
- What is the MOSFET switching frequency?
- What is the output voltage value?
- How large the control signal amplitude should be if the output voltage value should be half of the previous value? What would be the duty cycle D value?



Example solution

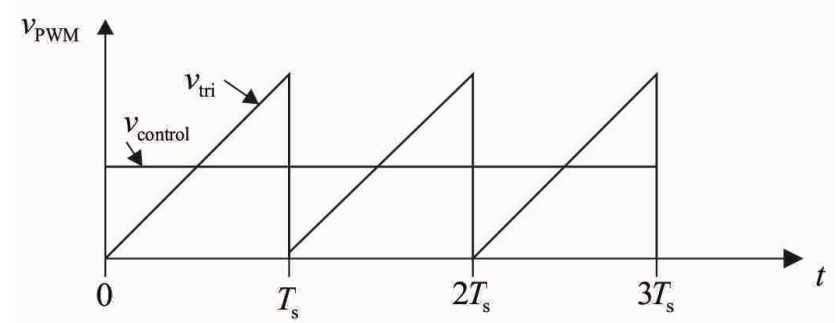

- a) What is the duty cycle D of the converter?

$$D = \frac{v_{control}}{v_{tri}} = \frac{1,2V}{3V} = 0,4$$

- a) What is the MOSFET switching frequency?

$$f_{sw} = \frac{1}{T_s} = \frac{1}{10\mu s} = 100kHz$$

- a) What is the output voltage value?

$$V_{out} = DV_{in} = 0,4 \cdot 50V = 20V$$

- b) How large the control signal amplitude should be if the output voltage value should be half of the previous value? What would be the duty cycle D value?

$$D = \frac{V_{out}}{V_{in}} = \frac{10V}{50V} = 0,2$$

$$v_{control} = Dv_{tri} = 0,2 \cdot 3V = 0,6V$$

